



University of Engineering and Management
Institute of Engineering & Management, New Town Campus
Department of Computer Science & Engineering



Computer Organization & Architecture Laboratory
PCCCS492

EXPERIMENT NO.:

TITLE: Realization of Boolean Expressions
Using Basic Gates (IC Chips).

OBJECTIVE: To realize of Boolean Expressions Using Basic Gates (IC Chips).

THEORY:

Logic expressions:

Using Basic Gates (IC Chips).

OBJECTIVE: To realize of Boolean Expressions Using Basic Gates (IC Chips).

THEORY:

Logic expressions:

i) $Y = A'B + C$

ii) $Y = AB' + C(A'+D)$

Computer Organization & Architecture Laboratory

PCCCS492

LOGIC DIAGRAM:

i)

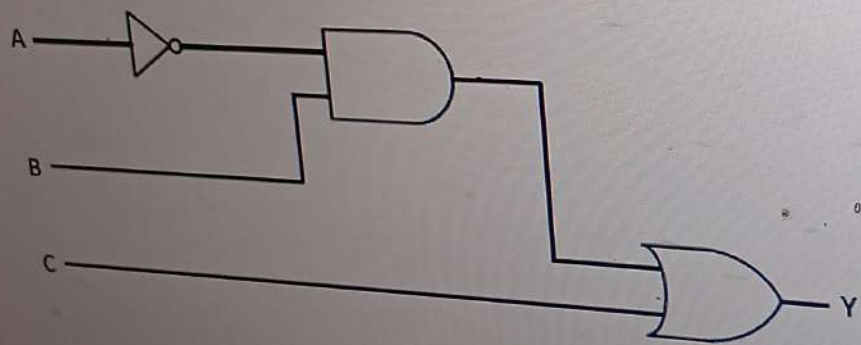


Fig : Logic Diagram for the expression of $Y = A'B + C$


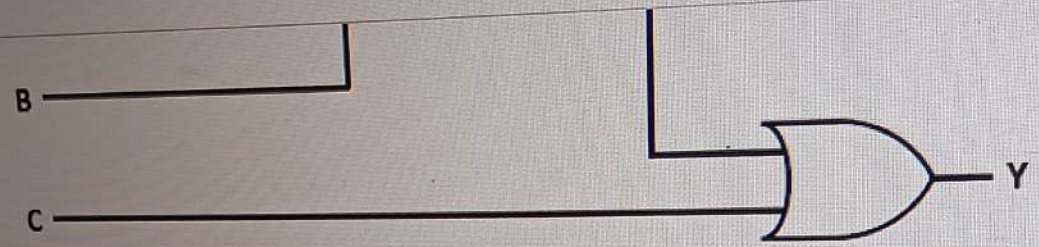


Fig : Logic Diagram for the expression of $Y = A'B + C$

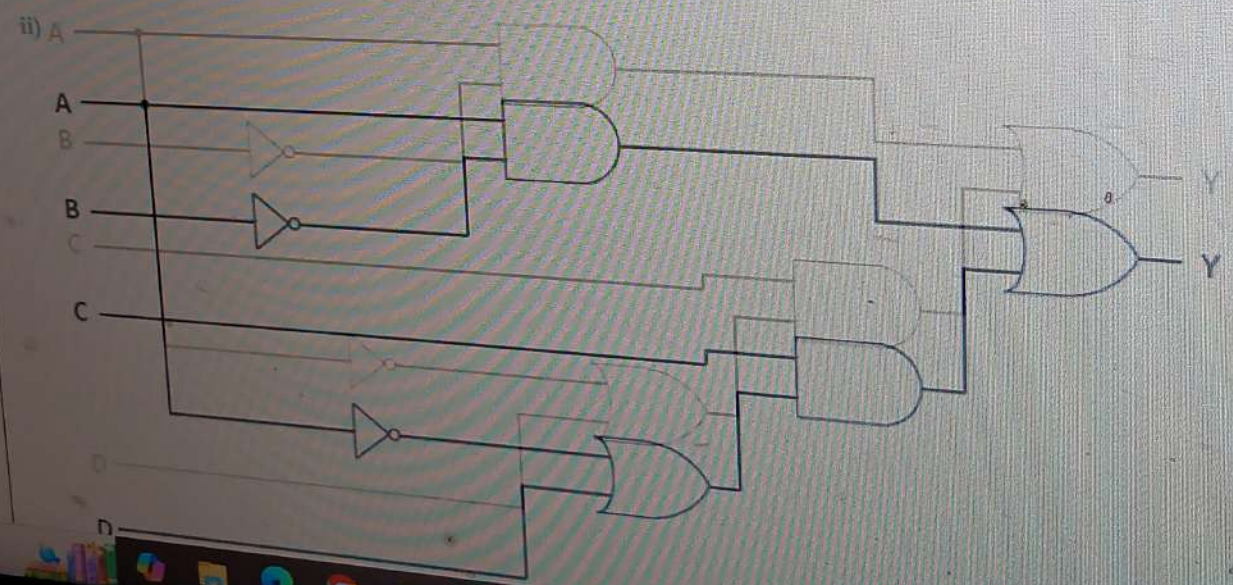

University of Engineering and Management
Institute of Engineering & Management, New Town Campus
Department of Computer Science & Engineering
PCCCS492
Computer Organization & Architecture Laboratory



Computer Organization & Architecture Laboratory

PCCCS492

ii)

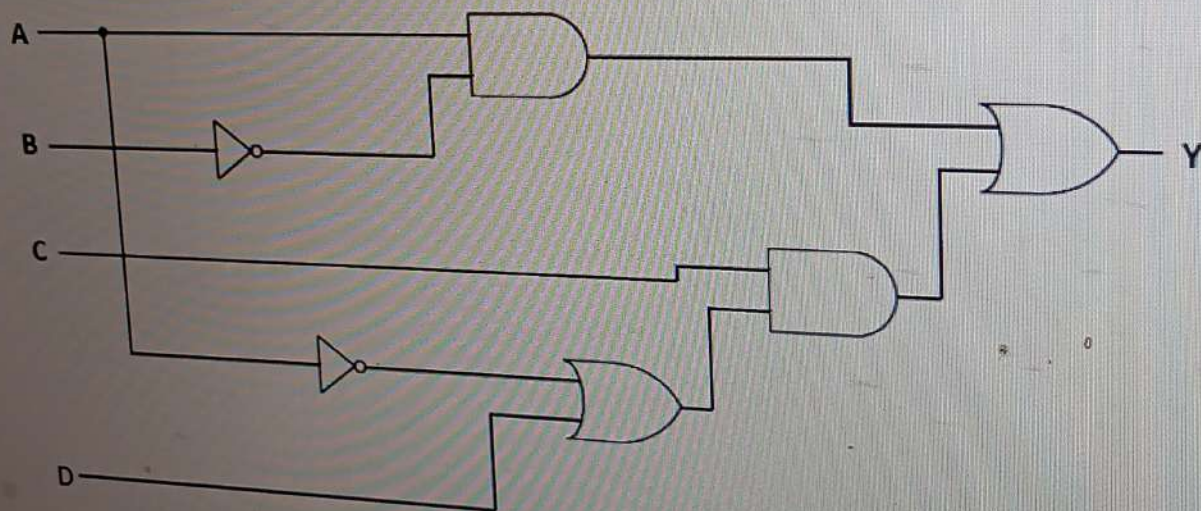


Fig : Logic Diagram for the expression of $Y = AB' + C(A' + D)$

INSTRUMENT & COMPONENT REQUIRED:

Computer Organization & Architecture Laboratory

PCCCS492

ii)

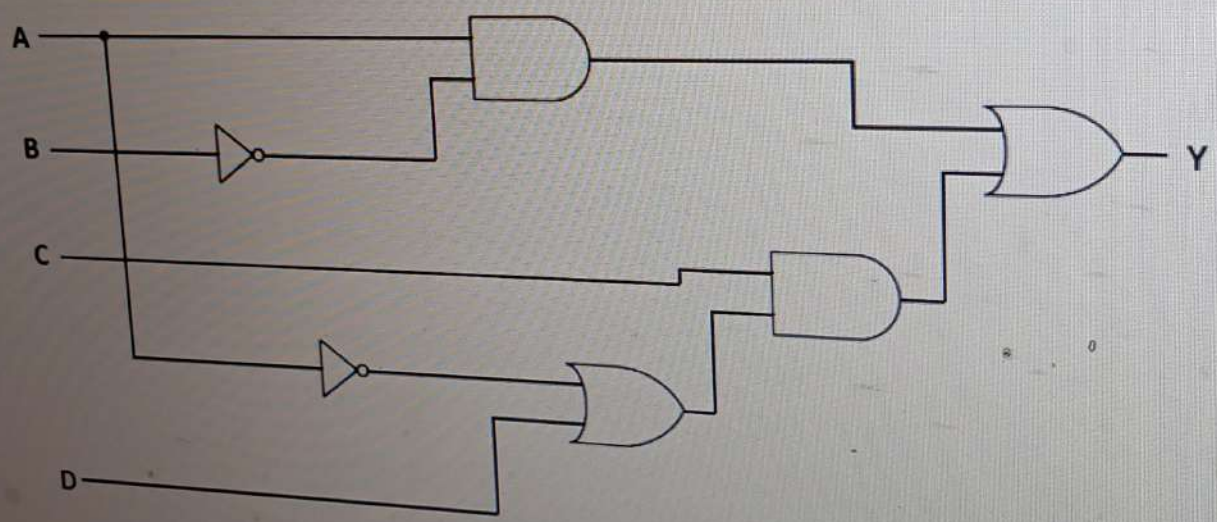


Fig : Logic Diagram for the expression of $Y = AB' + C(A' + D)$

INSTRUMENT & COMPONENT REQUIRED:



E-Sign

D

Fig : Logic Diagram for the expression of $Y = AB' + C(A'+D)$

INSTRUMENT & COMPONENT REQUIRED:

Sl. No.	Item	Specification	Qty.

VERIFICATION TABLE:

i) for the expression of $Y = A'B + C$

Input			Output
A	B	C	Y





ii) for the expression of $Y = AB' + C(A'+D)$

Input				Output
A	B	C	D	Y

CONCLUSION:





E-Sign

CONCLUSION: