

Design of A 4-Bit Parallel Binary Adder circuit Using The IC-Chip 4008

Click to odd subtitle

Introduction

-What is a Binary Adder?

A circuit that adds binary numbers.

-Importance of Binary Adders:

Used in ALUs, digital calculators, and data processing.

-Introduction to IC 4008:

4-bit full adder IC.

High-speed binary addition with cascading support.

L

IC4008 overview

-Key Features:

• 4-bit parallel addition.

• Accepts carry-in and generates carry-out.

• Operates within 5V to 15V.

(-SV)

vDD

Cout

22

IC
4008

AEAGUtPut

Cin

GNO

in Diagram

A3
B2
A2
B1
A1
GND

4
5
7
8

4008

16 V_{oo}
15 B4
14 C_{ouT}
13 s4
12 s3
11 s2
10 s
9 G

VERIFIC ATION TABLE

Input (A				Input (B)	Output (s)		
A	Ag	As	Ba	B	S	S	S