



**University of Engineering & Management, Kolkata**

**Subject Name: Computer Organization & Architecture Laboratory**

**Subject Code: PCCCS492**

### **ASSIGNMENT – 8**

**8.1. TITLE:** Implementation of 4:1 MUX using 2:1 MUX (using Structural Method) in VHDL.

#### **8.2. APPARATUS REQUIRED:**

- a. ModelSim software.

#### **8.3. THEORY:**

A multiplexer (or mux), also known as a data selector, is a device that selects between several analog or digital input signals and forwards the selected input to a single output line. The selection is directed by a separate set of digital inputs known as select lines. A multiplexer of  $2^n$  inputs has  $n$  select lines, which are used to select which input line to send to the output.

##### **8.3.1. TRUTH TABLE FOR 4:1 MULTIPLEXER:**

<b>E</b>	<b>Select</b>		<b>Input</b>				<b>Output</b>
	<b>S<sub>1</sub></b>	<b>S<sub>0</sub></b>	<b>D<sub>3</sub></b>	<b>D<sub>2</sub></b>	<b>D<sub>1</sub></b>	<b>D<sub>0</sub></b>	<b>Y</b>
0	×	×	×	×	×	×	0
1	0	0	×	×	×	1	1
1	0	1	×	×	1	×	1
1	1	0	×	1	×	×	1
1	1	1	1	×	×	×	1


### 8.3.2. K-MAP FOR OUTPUT OF 4:1 MULTIPLEXER:

K-Map for Output:


$S_1 S_0$		00	01	11	10
E	0	0	0	0	0
	1	$D_0$	$D_1$	$D_3$	$D_2$

$$Y = \overline{E} \overline{S_1} \overline{S_0} D_0 + \overline{E} \overline{S_1} S_0 D_1 + E \overline{S_1} \overline{S_0} D_2 + E \overline{S_1} S_0 D_3$$
 
### 8.3.3. 4:1 MULTIPLEXER USING BASIC GATES:



### 8.3.4. 4:1 MUX USING 2:1 MUX:

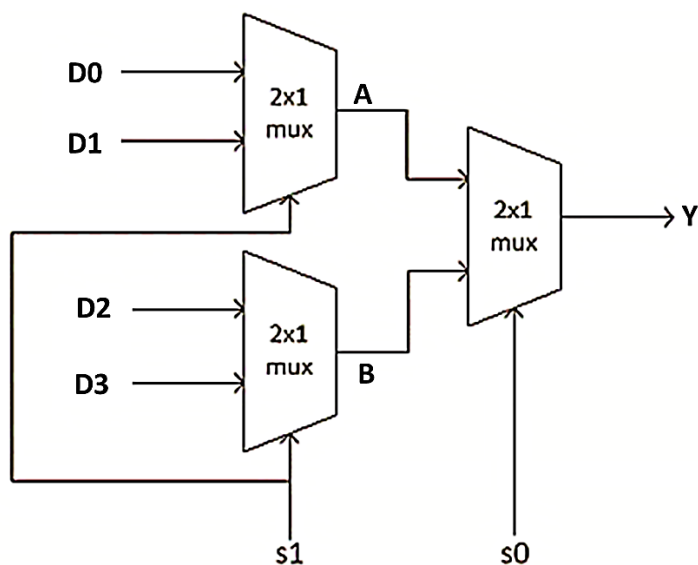

## 8.4. VHDL CODE:

### 8.4.1. Component 2:1 MUX (using Behavioral Method):

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;


entity MUX2_3 is
port(P,Q : in STD_LOGIC;
S: in STD_LOGIC;
R: out STD_LOGIC);
end MUX2_3;

architecture BEHAVIORAL of MUX2_3 is


begin

process (P,Q,S) is
begin
if (S ='0') then
R <= P;
else
R <= Q;
end if;
end process;

end BEHAVIORAL;
```

 

### 8.4.2. Testbench waveform:

 

### 8.4.3. 4:1 MUX using 2:1 MUX (using Structural Method):

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MUX4_2 is
port(D0,D1,D2,D3 : in STD_LOGIC;
     S0,S1: in STD_LOGIC;
     Y: out STD_LOGIC);
end MUX4_2;

architecture STRUCTURAL of MUX4_2 is

component MUX2_3 is
port(P,Q : in STD_LOGIC;
     S: in STD_LOGIC;
     R: out STD_LOGIC);
end component;

signal A, B: std_logic;
```


```

begin
m1: MUX2_3 port map(D0,D1,S1,A);
m2: MUX2_3 port map(D2,D3,S1,B);
m3: MUX2_3 port map(A,B,S0,Y);

end STRUCTURAL;

```

#### 8.4.4. Testbench waveform:

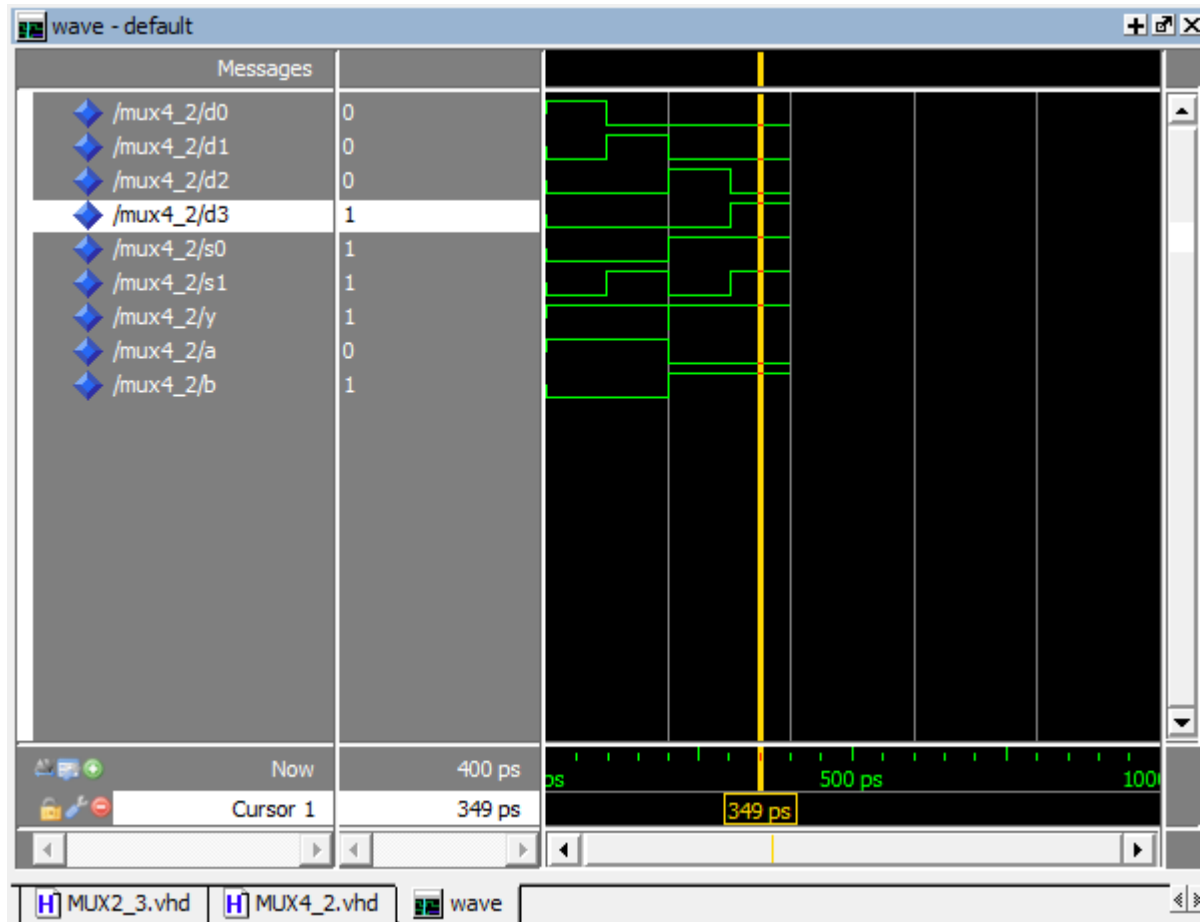

#### 8.5. PROCEDURE:

- I. Create a new project in ModelSim platform.
- II. Create a new file under this project.
- III. Write the VHDL code in the editor window.
- IV. Save and compile the written code.
- V. Simulate the code and generate the testbench waveform.

#### 8.6. CONCLUSION: