

### Experiment-3

Realisation of Parallel adder using IC 4008.

Aim: To realise parallel adder using IC 4008.

Theory: A digital circuit that adds two binary numbers of any bit length in parallel form and produces the sum of these numbers in parallel form is called a parallel adder.

⇒ A parallel adder basically consists of full adders in a chain form.

⇒ Here, the output bit of each full adder is connected to the input carry terminal of the next full adder circuit in the chain.


Working Principle of Parallel Adder:

The parallel adder performs the binary addition of two numbers as per the following step:

Step 1: Firstly the full adder circuit FA<sub>1</sub>, adds the bits A<sub>1</sub> and B<sub>1</sub> along with the input carry bit C<sub>in</sub> to produce the sum bit S<sub>1</sub>, where it is the LSB of the output sum. At this stage,

Teacher's Signature .....



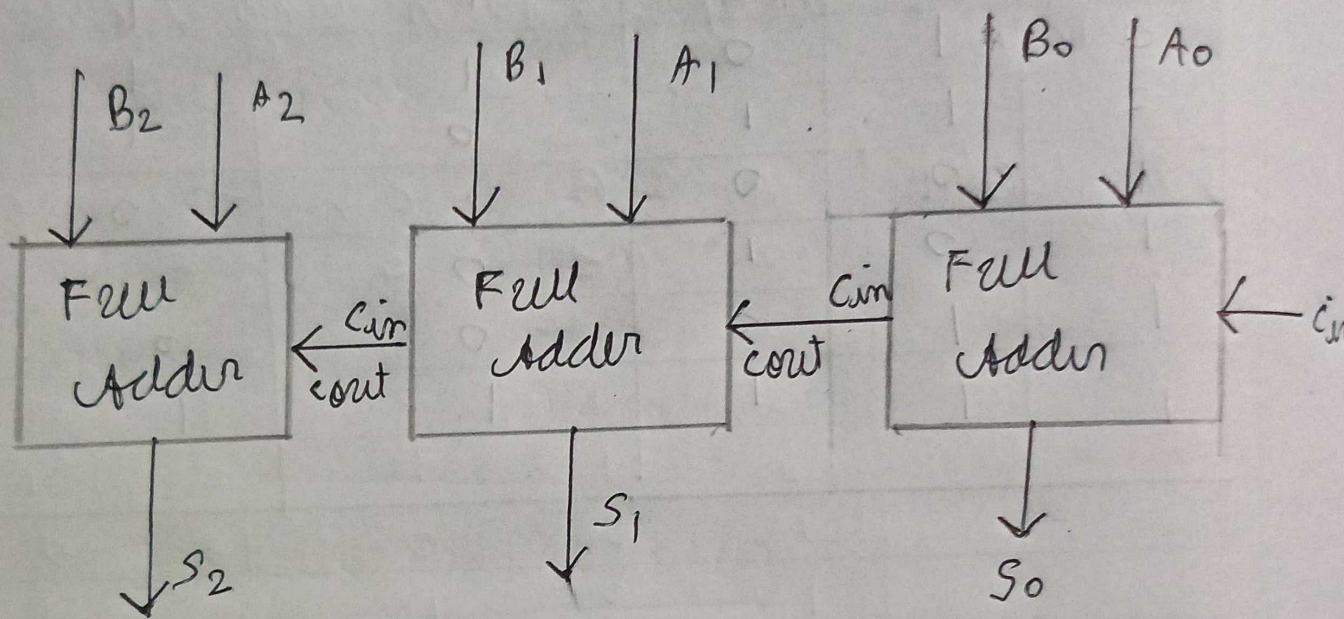

Block diagram of 3-bit parallel adder




a carry bit  $C_1$  is generated which is transferred to the next full adder circuit in the chain.

Step 2: The full adder circuit  $FA_2$  adds bits  $A_2$  and  $B_2$  along with the carry bit  $C_1$  from the previous addition. It produces the sum bit  $S_2$  which is the second bit of the output sum, and a carry bit  $C_2$  is also produced which is again forwarded to the next full adder  $FA_3$ .

Step 3: The full adder circuit  $FA_3$  adds input bits  $A_3$  and  $B_3$  along with the carry bit  $C_2$  from previous addition to produce sum bit  $S_3$  and carry bit  $C_3$ .

Step 4: The full adder circuit  $FA_4$  adds input bits  $A_4$  and  $B_4$  along with the carry bit  $C_3$  forward from  $FA_3$ . It generates the last sum bit  $S_4$  and a last carry bit  $C_4$ .

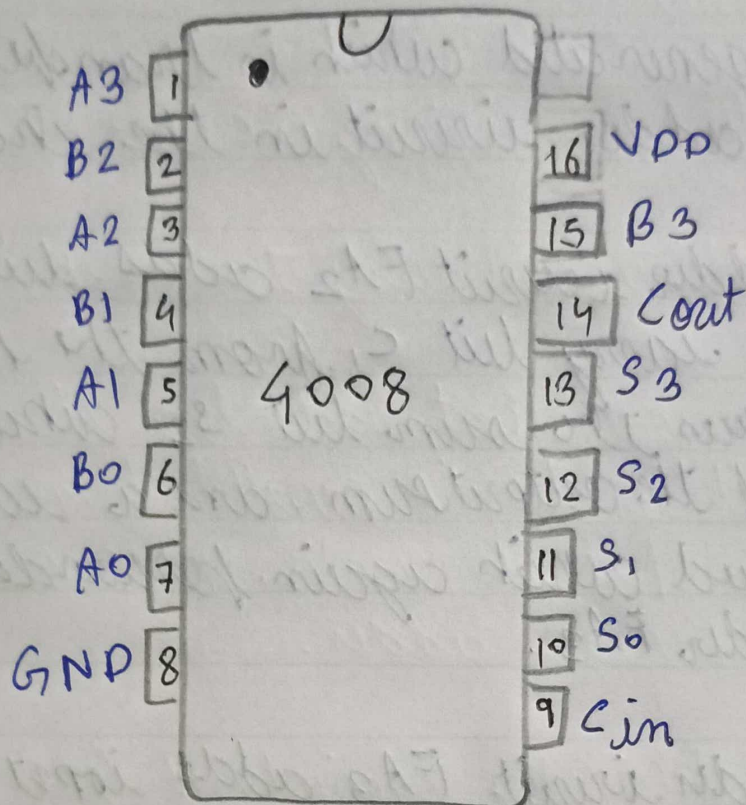Step 5: The output sum of the parallel adder is then given by  $S_{out} = C_4 S_4 S_3 S_2 S_1$



IC 4008 Parallel Adder



## Constructing a Parallel Adder

- 1) The A0 to A3 pins are the inputs for the 4 bits of the number A.
- 2) The B0 to B3 pins are the inputs for the 4 bits of number B.
- 3) The Cin pin is the input for a carry in bit. It's only used if you are combining several adders. Set to Low when not in used.
- 4) The S0 to S3 pins are the outputs for the 4 bits of the sum S.
- 5) The Cout pin is the output for the 5th bit of the sum S (or carry out bit)

### Pin Overview:

Pin Name	Pin #	Type	Description
VDD	16	Power	Supply Voltage (+3 to +5V)

Teacher's Signature .....



GND	8	Power	Ground (0V)
A <sub>0</sub> to A <sub>3</sub>	7, 5, 3, 1	Input	Bits 0 to 3 for input number A
B <sub>0</sub> to B <sub>3</sub>	6, 4, 2, 13	Input	Bits 0 to 3 for input number B
C <sub>IN</sub>	9	Input	Carry-In bit
S <sub>0</sub> to S <sub>3</sub>	10, 11, 12, 13	Output	Bits 0 to 3 for output sum
cout	14	Output	Carry Out Bit (Bit 4)

Conclusion :

Consider an example of  $(100)_2 + (011)_2$

Here,  $X = 100$  ( $X_2 = 1, X_1 = 0, X_0 = 0$ )

$Y = 011$  ( $Y_2 = 0, Y_1 = 1, Y_0 = 1$ )

In 1st Full Adder,

Teacher's Signature .....

$$S_0 = X_0 + Y_0 + C_{in} = 0 + 1 + 0 = 1$$
$$C_0 = 0$$

In 2nd full adder,

$$S_1 = X_1 + Y_1 + C_0 = 0 + 1 + 0 = 1$$
$$C_1 = 0$$

In 3rd full adder,

$$S_2 = X_2 + Y_2 + C_1 = 1 + 0 + 0 = 1$$
$$C_2 = 0$$

Thus,  $X = 100 = 4$

$$Y = 011 = 3$$

$$\text{Sum} = 0111 = 7$$