



University of Engineering & Management, Kolkata

Subject Name: Computer Organization & Architecture Laboratory

Subject Code: PCCCS492

ASSIGNMENT – 6

6.1. TITLE: Implementation of Full Adder using VHDL (Dataflow and Behavioral Model).

6.2. APPARATUS REQUIRED:

- a. ModelSim software.

6.3. THEORY:

A full adder adds binary numbers and accounts for values carried in as well as out. A one-bit full adder adds three one-bit numbers, often written as A, B, and C_{in} ; A and B are the operands, and C_{in} is a bit carried in from the previous less-significant stage. The circuit produces a two-bit output such as sum (S) and carry (C_{out}).

6.3.1. TRUTH TABLE FOR FULL ADDER:

Input			Output	
A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

6.3.2. K-MAP FOR SUM AND CARRY FOR FULL ADDER:

K-Map for sum:

		BC _{in}			
		00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0


$S = A \oplus B \oplus C_{in}$

K-Map for carry:

		BC _{in}			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

$C_{out} = AB + AC_{in} + BC_{in}$

6.3.3. FULL ADDER USING BASIC GATES:

 

6.3.4. VHDL CODE:

6.3.4.1. Dataflow Model:

```
library IEEE;
use IEEE.std_logic_1164.all;

-- Entity declaration

entity FA_DATAFLOW_1 is

    port(A : in std_logic;    -- FA input
         B : in std_logic;    -- FA input
         CIN : in std_logic;  -- FA input
         SUM : out std_logic; -- FA output
         CARRY : out std_logic); -- FA output

end FA_DATAFLOW_1;

-- Dataflow Modelling Style
-- Architecture definition
```

architecture DATAFLOW of FA_DATAFLOW_1 is


begin

SUM <= A XOR B XOR CIN;

CARRY <= (A AND B) OR (A AND CIN)OR (B AND CIN);

end DATAFLOW;

6.3.4.2. Testbench waveform:

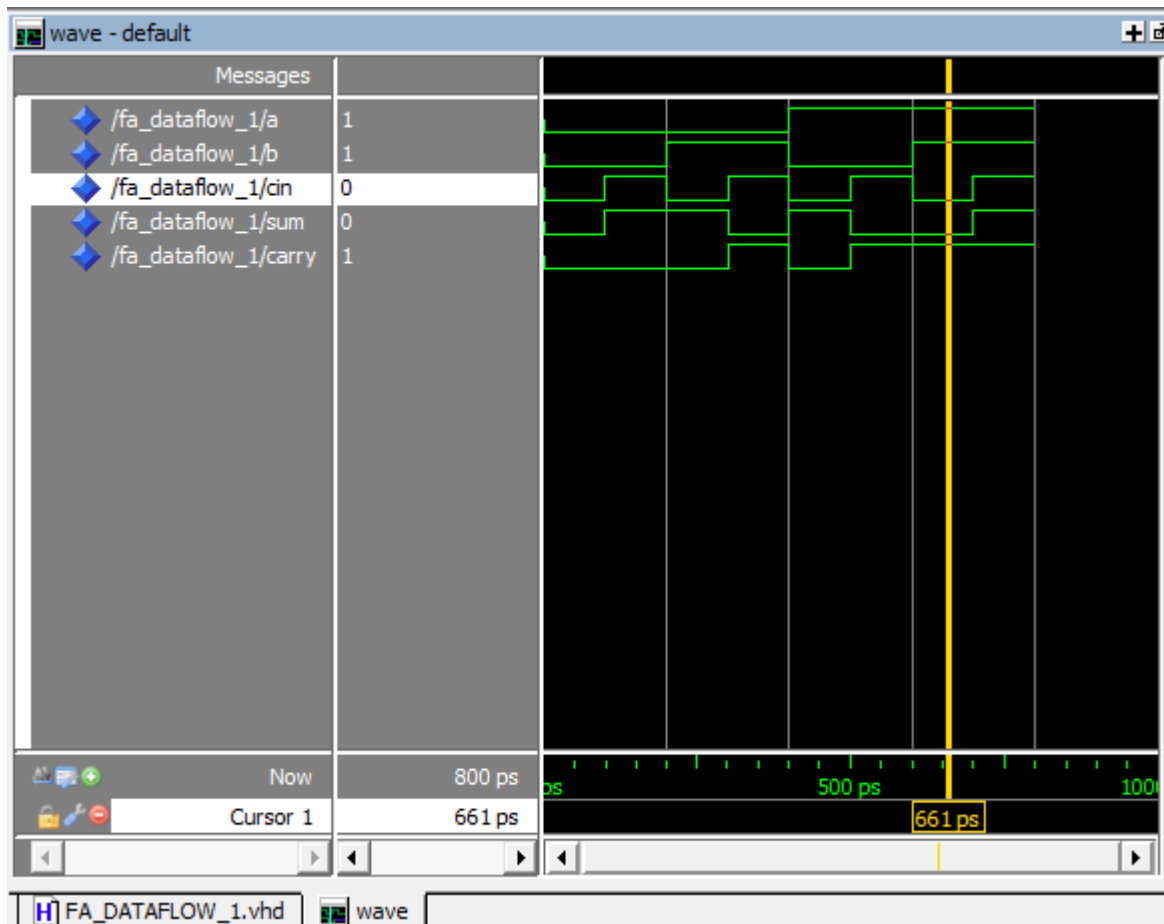

6.3.4.3. Behavioral Model:

library IEEE;

use IEEE.std_logic_1164.all;

-- Entity declaration

entity FA_BEHAVE_2 is

port(A : in std_logic; -- FA input

```

        B : in std_logic;    -- FA input
        CIN : in std_logic;  -- FA input
        SUM : out std_logic; -- FA output
        CARRY : out std_logic); -- FA output

end FA_BEHAVE_2;

-- Behavioural Modelling Style
-- Architecture definition

architecture BEHAVIOURAL of FA_BEHAVE_2 is
begin
    process (A,B,CIN)
    begin

        if A = '0' then
            if B = '0' then
                SUM <= CIN;
                CARRY <='0';

            else

                SUM <= not CIN;
                CARRY <= CIN;

            end if;

        else

            if B = '0' then

                SUM <= not CIN;
                CARRY <= CIN;

            else

                SUM <= CIN;
                CARRY <='1';

            end if;


        end if;

    end process;

end BEHAVIOURAL;

```

6.3.4.4. Testbench waveform:

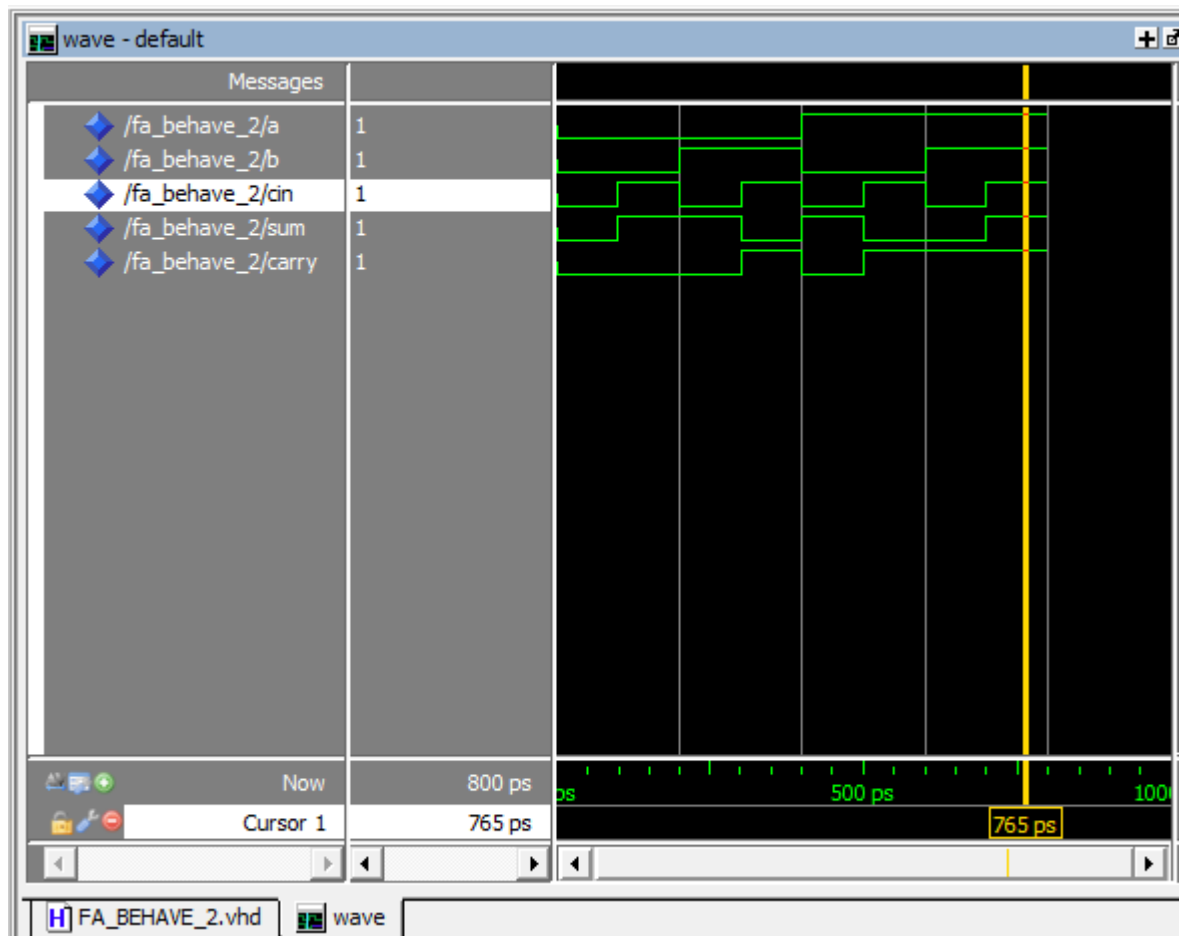

6.4. PROCEDURE:

- I. Create a new project in ModelSim platform.
- II. Create a new file under this project.
- III. Write the VHDL code in the editor window.
- IV. Save and compile the written code.
- V. Simulate the code and generate the testbench waveform.

6.5. CONCLUSION: