

University of Engineering and Management
Institute of Engineering & Management, New Town Campus
Department of Computer Science & Engineering

Computer Organization & Architecture Laboratory
PCCCS492



EXPERIMENT NO.:

TITLE: Implementation of Half Adder, Half Subtractor, Full Adder, Full Subtractor using VHDL (Dataflow model).

OBJECTIVE: To implement of Half Adder, Half Subtractor, Full Adder, Full Subtractor using VHDL (Dataflow model).

Ask AI Assistant

Subtractor, Full Adder, Full Subtractor using VHDL (Dataflow model).

OBJECTIVE: To implement of Half Adder, Half Subtractor, Full Adder, Full Subtractor using VHDL (Dataflow model).

THEORY:

Half Adder

Half adder is a combinational logic circuit with two inputs and two outputs. The half adder circuit is designed to add two single bit binary number A and B. It is the basic building block for addition of two single bit numbers. This circuit has two outputs carry and sum.

$$S = A'B + AB'$$

$$C = AB$$

Department of Computer Science & Engineering
Computer Organization & Architecture Laboratory
PCCCS492

Block diagram



Truth Table

INPUT		OUTPUT	
A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Full Adder

Full adder is developed to overcome the drawback of Half Adder circuit. It can add two one-bit numbers A and B, and carry c. The full adder is a three input and two output combinational circuit.

$$\text{Sum} = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$




Full adder is developed to overcome the drawback of Half Adder circuit. It can add two one-bit numbers A and B, and carry c. The full adder is a three input and two output combinational circuit developed to overcome the drawback of Half Adder circuit. It can add two one-bit numbers A and B, and carry c. The full adder is a three input and two output combinational circuit.

$$\text{Sum} = \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}\overline{C}_{in} + ABC_{in}$$

$$C_{out} = AB + A\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + ABC_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

Block diagram

 

Truth Table

INPUT			OUTPUT	
A	B	C _{in}	C _{out}	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1




Full adder is developed to overcome the drawback of Half Adder circuit. It can add two one-bit numbers A and B, and carry c. The full adder is a three input and two output combinational circuit.

$$\text{Sum} = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

Block diagram

 

Truth Table

INPUT			OUTPUT	
A	B	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

Half Subtractor

Half subtractor is a combination circuit with two inputs and two outputs (difference and borrow). It produces the difference between the two binary bits at the input and also produces an output (Borrow) to indicate if a 1 has been borrowed. In the subtraction (A-B), A is called as Minuend bit and B is called as Subtrahend bit.

$$\text{Difference} = A \oplus B$$

$$\text{Borrow} = \bar{A}B$$

Block diagram



Truth Table

INPUT		OUTPUT	
A	B	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

PCCCS492


Full Subtractor

The disadvantage of a half subtractor is overcome by full subtractor. The full subtractor is a combinational circuit with three inputs A,B,Bin and two output D and Bout. A is the 'minuend', B is 'subtrahend', Bin is the 'borrow' produced by the previous stage, D is the difference output and Bout is the borrow output.

$$D=A'B'Bin + AB'Bin' + A'BBin' + ABBin$$

$$Bout=A'Bin + A'B + BBin$$

Block diagram

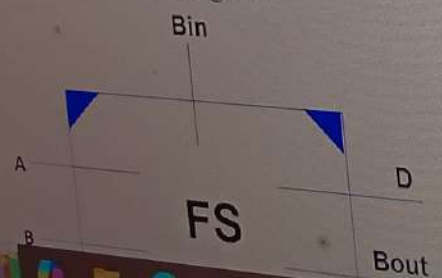

Truth Table

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0


Full Subtractor

The disadvantage of a half subtractor is overcome by full subtractor. The full subtractor is a combinational circuit with three inputs A,B,Bin and two output D and Bout. A is the 'minuend', B is 'subtrahend', Bin is the 'borrow' produced by the previous stage, D is the difference output and Bout is the borrow output.

$$D = A'B'Bin + AB'Bin' + A'BBin' + ABBin$$

$$Bout = A'Bin + A'B + BBin$$

Block diagram

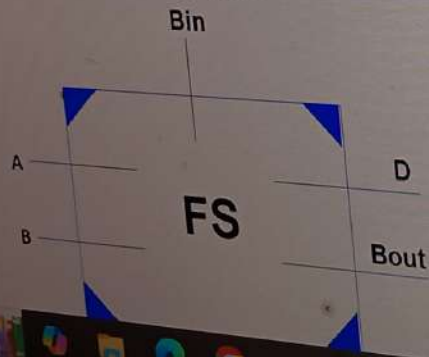


Truth Table

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$Bout = A'Bin + A'B + BBin$$

Block diagram

 


Truth Table

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0 ⁰
1	1	1	1	1



Block diagram

 

Truth Table

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1



PROBLEM STATEMENT:

1. Write a VHDL program for a Half adder using the dataflow modeling style.
2. Write a VHDL program for a Half Subtractor using the dataflow modeling style.
3. Write a VHDL program for a Full Adder using the dataflow modeling style.
4. Write a VHDL program for a Full Subtractor using the dataflow modeling style.

SOFTWARE USED:

CO_Lab_logic expression_exp3_

☆ CA_Lab_HAHS,FA,FS_e x

+ Create

Find text or tools



Convert E-Sign

SOFTWARE USED:

Type here to search



PCCCS492

PROGRAM:

1. Half adder:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity half_adder is
```

```
    port(a,b:in bit; sum,carry:out bit);
```

```
end half_adder;
```

```
architecture data of half_adder is
```

```
begin
```

```
    sum<= a xor b;
```

```
    carry <= a and b;
```

```
end data;
```



```
port(a,b:in bit; sum,carry:out bit);  
end half_adder;
```

architecture data of half_adder is

begin

```
sum<= a xor b;
```

```
carry <= a and b;
```

```
end data;
```

2. Half-Subtractor:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```



```
carry <= a and b;  
end data;
```

2. Half-Subtractor:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;



University of Engineering and Management
Institute of Engineering & Management, New Town Campus
Department of Computer Science & Engineering
Computer Organization & Architecture





entity half_sub is

port (a,b : in std_logic;

dif,bo: out std_logic);

end half_sub;

architecture sub_arch of half_sub is

begin

dif <= a xor b;

bo <= (not a) and b;

end sub_arch;

3. Full adder:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;



3. Full adder:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity full_adder is port

(a,b,c:in bit; sum,carry:out bit);

end full_adder;

architecture data of full_adder is



```
begin
```

```
sum<= a xor b xor c;
```

```
carry <= ((a and b) or (b and c) or (a and c));
```

```
end data;
```

4. Full-Subtractor :

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity full_sub is
```

```
port (A,B,Bm: in std_logic;
```

```
D, Bout: out std_logic);
```

```
end full_sub;
```



```
begin
```

```
sum<= a xor b xor c;
```

```
carry <= ((a and b) or (b and c) or (a and c));
```

```
end data;
```

4. Full-Subtractor :

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity full_sub is
```

```
port (A,B,Bin: in std_logic;
```

```
D, Bout: out std_logic);
```

```
end full_sub;
```




4. Full-Subtractor :

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity full_sub is

port (A,B,B_{in}: in std_logic;

D, B_{out}: out std_logic);

end full_sub;

architecture data of full_sub is

begin

D <= A xor B xor B_{in};

B_{out} <= ((NOT(A) and B_{in}) or (NOT(A) and B) or (B and B_{in}));

end data;



```
carry <= ((a and b) or (b and c) or (a and c));  
end data;
```

4. Full-Subtractor :

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity full_sub is
```

```
    port (A,B,Bin: in std_logic;
```

```
          D, Bout: out std_logic);
```

```
end full_sub;
```

```
architecture data of full_sub is
```

```
begin
```

```
    D <= A xor B xor Bin;
```

```
    Bout <= ((NOT(A) and Bin) or (NOT(A) and B) or (B and Bin));
```

```
end data;
```


b_logic expression_exp3_

☆ CA_Lab_HA,HS,FA,FS_e_ x

+ Create

t E-Sign

Find text or tools



Sign in



University of Engineering and Management
Institute of Engineering & Management, New Town Campus
Department of Computer Science & Engineering



Computer Organization & Architecture Laboratory
PCCCS492

TIMING DIAGRAM:

CONCLUSION: